

VERILOG PROJECT

RISC-V



Smart Village
Main Branch

By:

Ahmed Ashraf El-HADY

September 9, 2023


Introduction: -

RISC-V is an open standard instruction set architecture (ISA) based on established reduced instruction set computer (RISC) principles.

Instruction format: -

Format	Bit																															
	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
Register/register	funct7							rs2				rs1				funct3			rd				opcode									
Immediate	imm[11:0]												rs1				funct3			rd				opcode								
Upper immediate	imm[31:12]																				rd				opcode							
Store	imm[11:5]							rs2				rs1				funct3			imm[4:0]				opcode									
Branch	[12]	imm[10:5]						rs2				rs1				funct3			imm[4:1]			[11]	opcode									
Jump	[20]	imm[10:1]										[11]	imm[19:12]						rd				opcode									

Design architecture: -

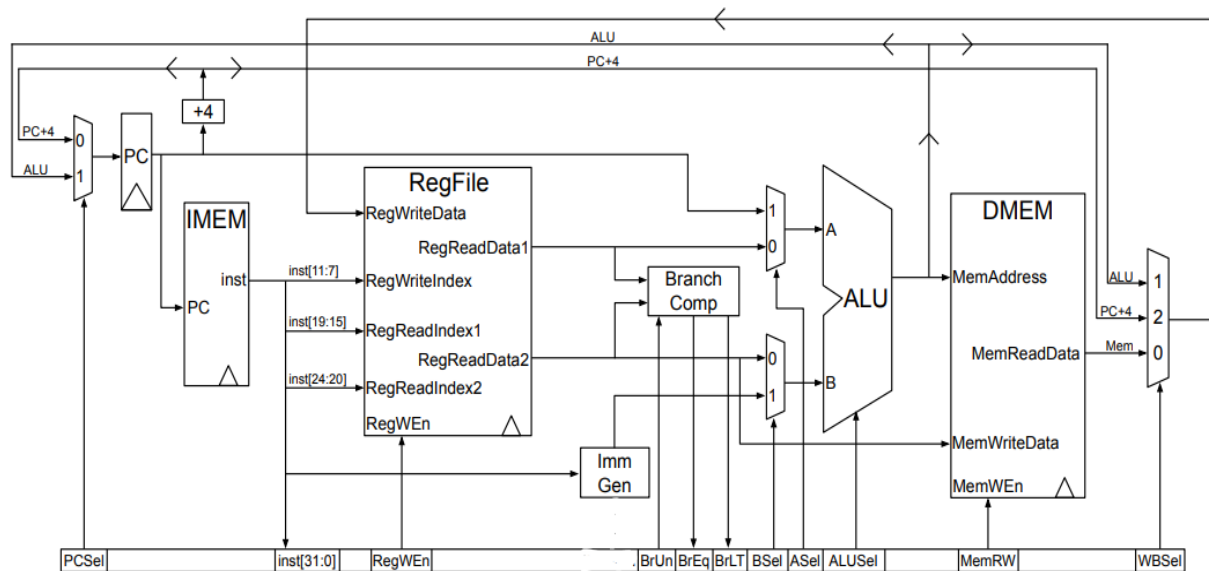

Covered instruction: -

[illegible]

Memory	lb	rd	imm(rs1)	Load Byte	rd = 1 byte of memory at address rs1 + imm, sign-extended	I	000	0011	000	
	lbu	rd	imm(rs1)	Load Byte (Unsigned)	rd = 1 byte of memory at address rs1 + imm, zero-extended	I	000	0011	100	
	lh	rd	imm(rs1)	Load Half-word	rd = 2 bytes of memory starting at address rs1 + imm, sign-extended	I	000	0011	001	
	lhu	rd	imm(rs1)	Load Half-word (Unsigned)	rd = 2 bytes of memory starting at address rs1 + imm, zero-extended	I	000	0011	101	
	lw	rd	imm(rs1)	Load Word	rd = 4 bytes of memory starting at address rs1 + imm	I	000	0011	010	
	sb	rs2	imm(rs1)	Store Byte	Stores least-significant byte of rs2 at the address rs1 + imm in memory	S	010	0011	000	
	sh	rs2	imm(rs1)	Store Half-word	Stores the 2 least-significant bytes of rs2 starting at the address rs1 + imm in memory	S	010	0011	001	
	sw	rs2	imm(rs1)	Store Word	Stores rs2 starting at the address rs1 + imm in memory	S	010	0011	010	

Control	beq	rs1 rs2 label	Branch if Equal	if (rs1 == rs2) PC = PC + offset	B	110 0011	000
	bge	rs1 rs2 label	Branch if Greater or Equal (signed)	if (rs1 >= rs2) PC = PC + offset	B	110 0011	101
	bgeu	rs1 rs2 label	Branch if Greater or Equal (Unsigned)	PC = PC + offset	B	110 0011	111
	blt	rs1 rs2 label	Branch if Less Than (signed)	if (rs1 < rs2) PC = PC + offset	B	110 0011	100
	bltu	rs1 rs2 label	Branch if Less Than (Unsigned)	PC = PC + offset	B	110 0011	110
	bne	rs1 rs2 label	Branch if Not Equal	if (rs1 != rs2) PC = PC + offset	B	110 0011	001
	jal	rd label	Jump And Link	rd = PC + 4 PC = PC + offset	J	110 1111	
	jalr	rd rs1 imm	Jump And Link Register	rd = PC + 4 PC = rs1 + imm	I	110 0111	000
	auipc	rd imm	Add Upper Immediate to PC	rd = PC + (imm << 12)	U	001 0111	
	lui	rd imm	Load Upper Immediate	rd = imm << 12	U	011 0111	

RTL analysis: -

```

module CPU (clk,rst,pc_m,pc,X,ins);
    input clk , rst;
    output[31:0] pc_m,X,ins;
    output reg [31:0]pc;

    wire [3:0]alu_sel;
    wire [2:0] pl_c;
    wire [1:0] wbsel;
    wire bsel,asel,we_r,brun,pcsel,brlt,breq;

```

```


        control_unit
cont(clk,alu_sel,bsel,wbsel,pl_c,we_r,asel,brun,breq,brlt,pcsel);

        data_bus
bus(clk,we_r,bsel,alu_sel,ins,wbsel,pl_c,asel,pcsel,brun,breq,brlt,p
c,pc_m,X);

        ins_mem insmem(clk,rst,pc,ins);

always @(posedge clk) begin
    if(rst) begin
        pc<= 0;
        $readmemh("reg_ini.mem",bus.regfile.r_f);
        $readmemh("Dmem_ini.mem",bus.d_mem.D_mem);
    end else begin
        pc <= pc_m;
    end
end
endmodule

```

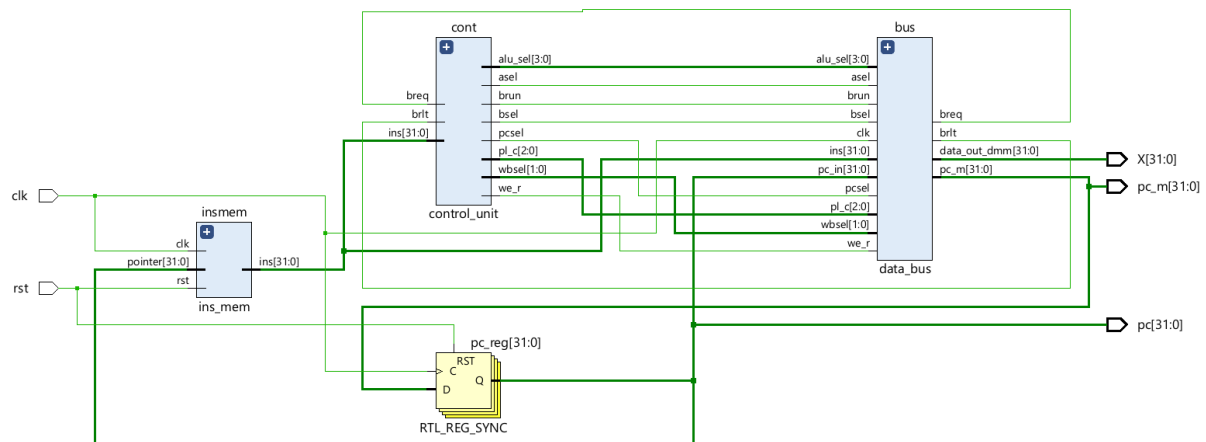

Instruction memory: -

```


// 1 KB ROM to keep ins
module ins_mem (clk,rst,pointer,ins);
input clk,rst;
input [31:0]pointer;
output [31:0] ins;
reg [31:0] ins_rom [255:0];

wire [7:0] add = pointer[9:2];

assign ins =ins_rom[add];

```

```
endmodule
```

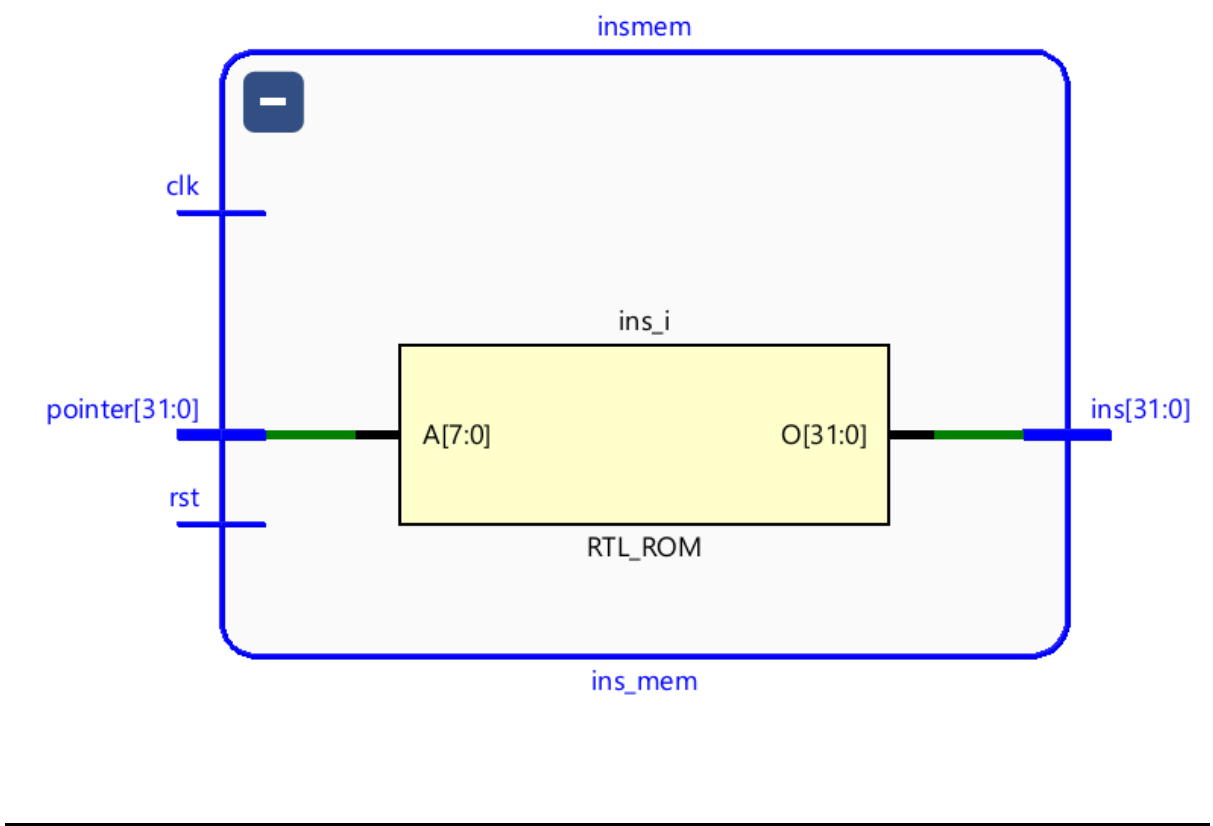

Control unit: -

[illegible]

```

input brlt, breq;
input [31:0] ins;
output reg [3:0] alu_sel;
output reg bsel, asel, we_r, brun, pcsel ;
output reg [1:0] wbsel;
output reg [2:0] pl_c;

wire [6:0] opcode;
wire [2:0] funct3;
wire [6:0] funct7;
assign opcode =ins[6:0];
assign funct3 =ins[14:12];
assign funct7 =ins[31:25];

//alu_sel
always @(*) begin
    bsel='bz;
    wbsel='bz;
    pl_c='bz;
    we_r='bz;
    asel='bz;
    brun='bz;
    pcsel='b0;
    if (opcode==7'h33)// Rtype Arth
        begin
            asel=0;
            pcsel=0;
            we_r=1;
            bsel=0;
            wbsel=2'h1;
            if (funct7==0)begin
                case (funct3)
                    'b000 : alu_sel= ADD;
                    'b001 : alu_sel= SLL;
                    'b010 : alu_sel= SLT;
                    'b011 : alu_sel=SLTU;
                    'b100 : alu_sel= XOR;
                    'b101 : alu_sel= SRL;
                    'b110 : alu_sel= OR ;
                    'b111 : alu_sel= AND;
                    default : alu_sel= 'bz;
                endcase
            end
            else if(funct7=='h20)begin
                if (funct3=='b101)
                    alu_sel= SRA;
                else if(funct3=='b000)
                    alu_sel= SUB;
            end
        end
end

```

```

        end
    else if(opcode==7'h13)// Itype Arth
        begin
            asel=0;
            ptsel=0;
            we_r=1;
            bsel=1;
            wbsel=2'h1;
            case (funct3)
                'b000 : alu_sel= ADD;
                'b001 : if(funct7==0)
                        alu_sel= SLL;

                'b010 : alu_sel= SLT;
                'b011 : alu_sel=SLTU;
                'b100 : alu_sel= XOR;
                'b101 :if(funct7==0)

                        alu_sel= SRL;
                        else
                        if(funct7=='h20)

                        alu_sel= SRA;
                'b110 : alu_sel= OR ;
                'b111 : alu_sel= AND;
                default : alu_sel= 'bz;
            endcase
        end
    else if(opcode==7'h03)// Itype MEM
        begin
            asel=0;
            ptsel=0;
            we_r=1;
            wbsel=2'h0;
            bsel=1;
            case (funct3)
                'b000 : begin alu_sel= ADD; pl_c =LB ;
                'b001 : begin alu_sel= ADD; pl_c =LH ;
                'b010 : begin alu_sel= ADD; pl_c =LW ;
                'b100 : begin alu_sel= ADD; pl_c
                =LBU; end
                'b101 : begin alu_sel= ADD; pl_c
                =LHU; end
                default : alu_sel= 'bz;
            endcase
        end
    end
end

```



```

        endcase

        end
    else if(opcode==7'h23)// Stype MEM
        begin
            asel=0;
            pcsel=0;
            we_r=0;
            bsel=1;
            case (funct3)
                'b000 : begin alu_sel= ADD; pl_c =SB ;
end
                'b001 : begin alu_sel= ADD; pl_c =SH ;
end
                'b010 : begin alu_sel= ADD; pl_c =SW ;
end
                default : alu_sel= 'bz;
            endcase

        end

    else if(opcode==7'h63)// Btype MEM
        begin
            case (funct3)
                'b000 : begin                if( breq
)begin alu_sel= ADD;asel=1; bsel=1;pcsel=1; end    end
                'b001 : begin                if(!breq
)begin alu_sel= ADD;asel=1; bsel=1;pcsel=1; end    end
                'b100 : begin brun=0; if( brlt )begin
alu_sel= ADD;asel=1; bsel=1;pcsel=1; end        end
                'b101 : begin        brun=0; if(!brlt )begin
alu_sel= ADD;asel=1; bsel=1;pcsel=1; end        end
                'b110 : begin        brun=1; if( brlt )begin
alu_sel= ADD;asel=1; bsel=1;pcsel=1; end        end
                'b111 : begin        brun=1; if(!brlt )begin
alu_sel= ADD;asel=1; bsel=1;pcsel=1; end        end
                default : begin brun=1'bz; alu_sel=
'bz;asel=1'bz; bsel=1'bz;pcsel=1'bz;    end
            endcase

        end

    else if(opcode==7'h67)// I type JALR
        begin
            if(funct3==0)begin
                wbsel=2'h2;
                we_r =1;
                bsel=1;
                asel=0;
                pcsel=0;

```

```

        alu_sel=ADD;
    end

    end

    else if(opcode==7'h6f)// J type    JAL
    begin
        ptsel=1;
        wtsel=2'h2;
        we_r =1;
        bsel=1;
        asel=1;
        alu_sel=ADD;

    end

    else if(opcode==7'h37)// U type    LUI
    begin

        ptsel=0;
        wtsel=2'h1;
        we_r =1;
        bsel=1;
        alu_sel=LUI;

    end

    else if(opcode==7'h17)// U type    AUIPC
    begin
        ptsel=0;
        wtsel=2'h1;
        we_r =1;
        bsel=1;
        asel=1;
        alu_sel=ADD;


    end


    end

end

endmodule

```

 

 

Data bus: -

```

module data_bus
(clk,we_r,bsel,alu_sel,ins,wbsel,pl_c,asel,pcsel,brun,breq,brlt,pc_i
n,pc_m,data_out_dmm);
    input clk,we_r,bsel,asel,brun,pcsel;
    input[1:0] wbsel;
    input [2:0] pl_c;
    input [3:0]alu_sel;
    input [31:0]ins,pc_in;
    output breq,brlt;
    output [31:0]pc_m,data_out_dmm;

    wire
[31:0]alu_out,r_d1,r_d2,r2_m,imm,reg_alu_out,lp_out,r1_m,pc_out,reg_
alu_out_m;
    pc_4 pc_plus(pc_in,pc_out);
    mux ux(pc_out,alu_out,pcsel,pc_m);
    reg_file
regfile(clk,we_r,ins[11:7],ins[19:15],ins[24:20],reg_alu_out,r_d1,r_


```



```


d2);
    alu alu_d(r1_m,r2_m,alu_sel,alu_out);
    mux B(r_d2,imm,bsel,r2_m);
    mux A(r_d1,pc_in,asel,r1_m);
    extend x(ins,imm);
    DMEM d_mem(clk,pl_c,alu_out,r_d2,data_out_dmm);
    //partial_load lp(data_out_dmm,pl_c,lp_out); // done inside
mem
    mux dmem_or_alu(data_out_dmm,alu_out,wbsel[0],reg_alu_out_m);
    mux mux_J(reg_alu_out_m,pc_out,wbsel[1],reg_alu_out);
    branch_comp comp(r_d1,r_d2,brun,breq,brlt);

endmodule

```

 

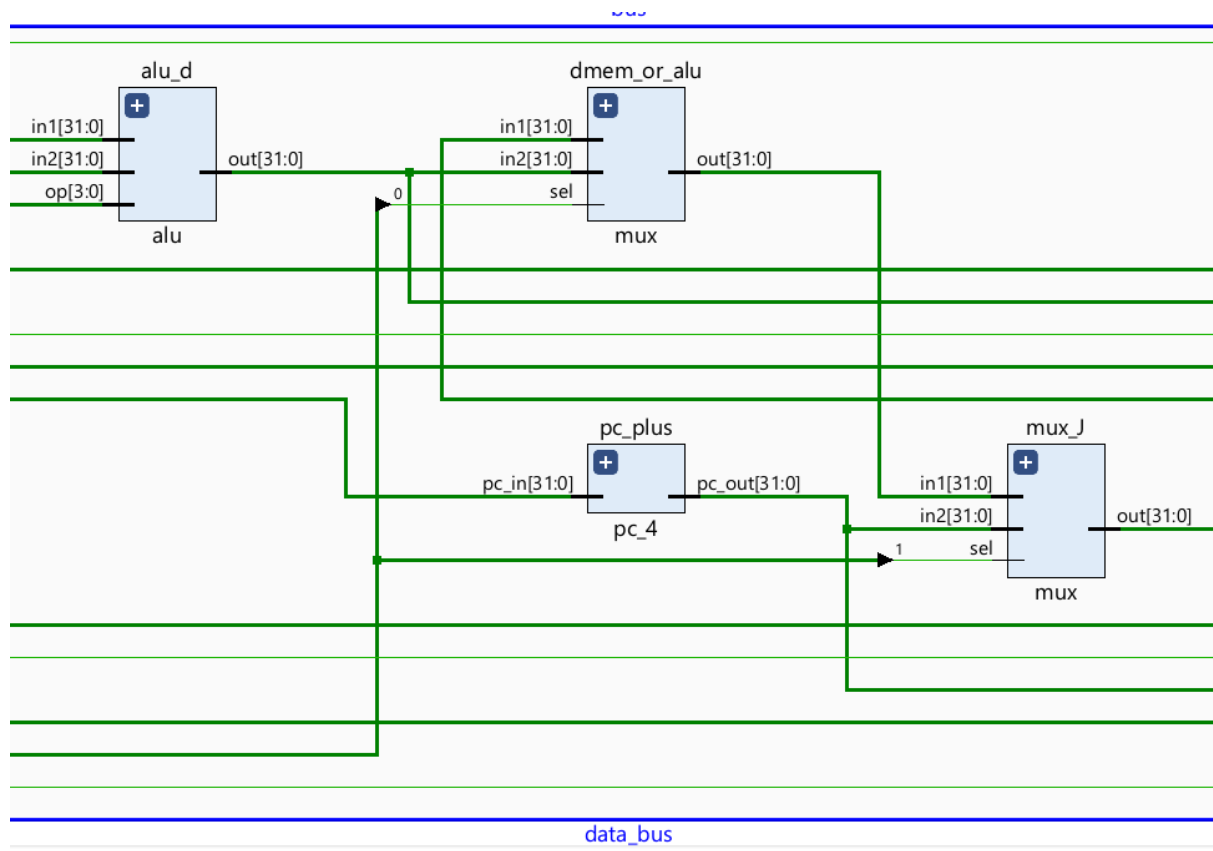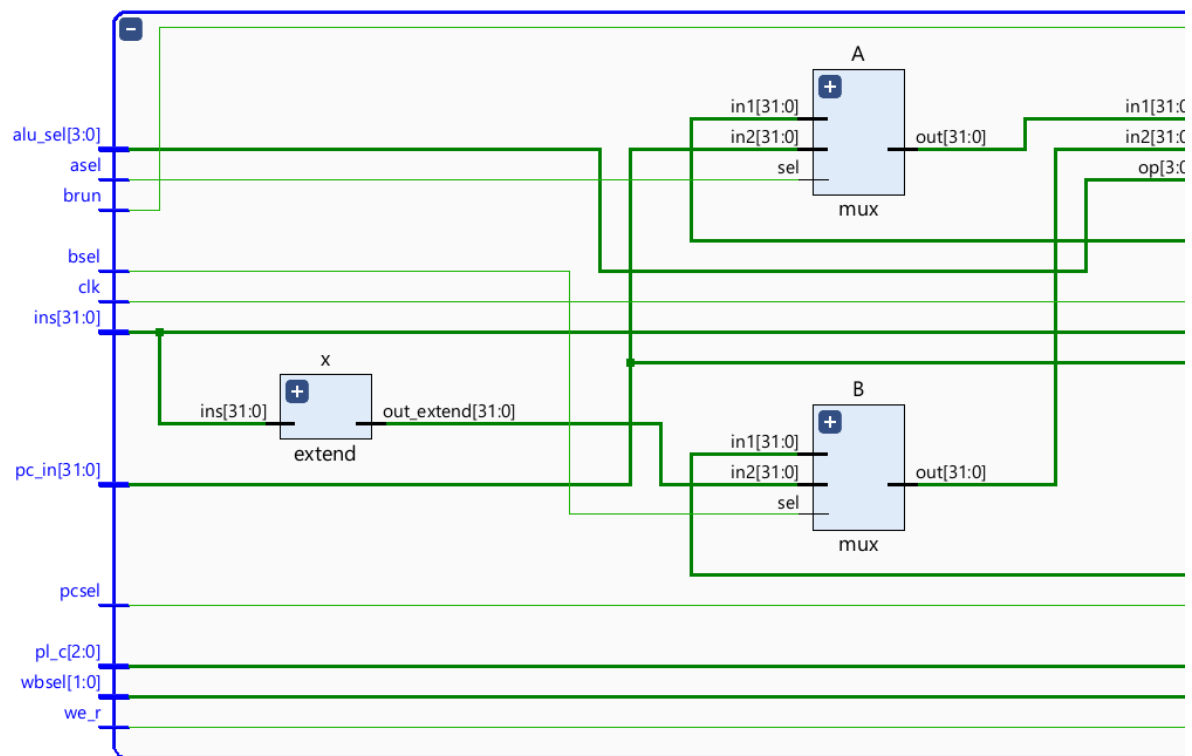

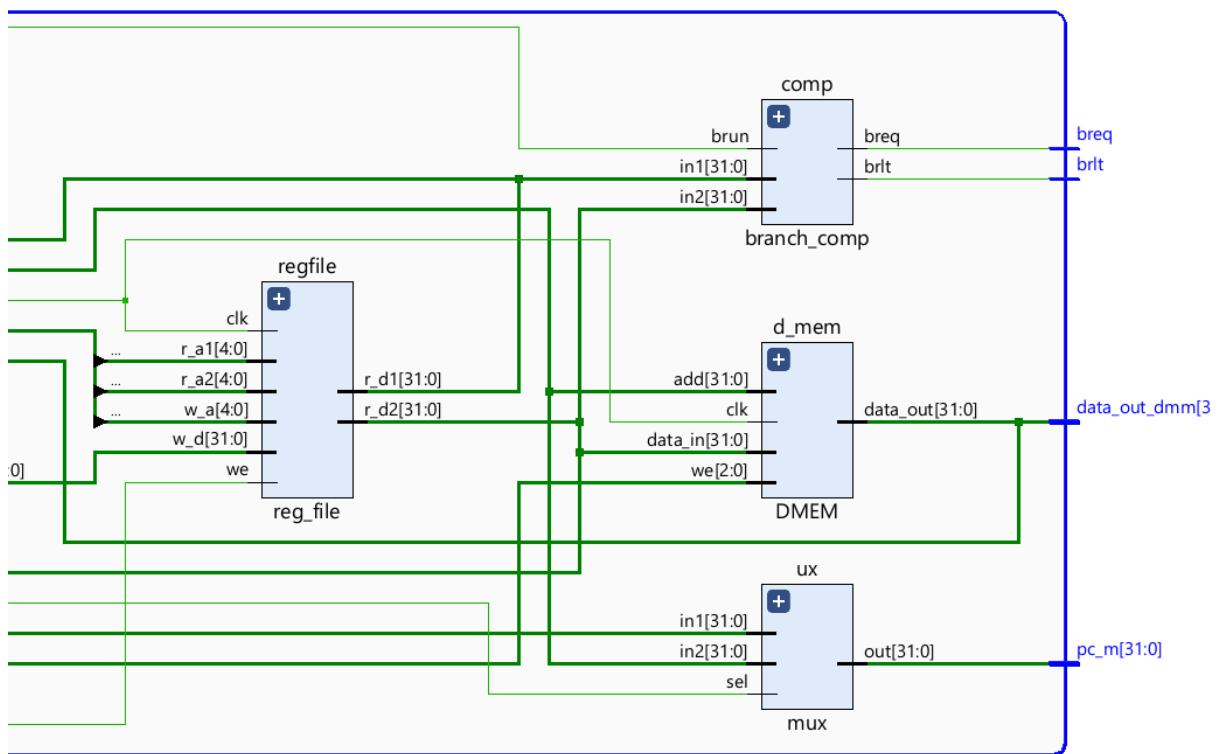

ALU: -

```
//operation can be performed : ADD SUB SLT SLTU _comapre signed and
unsigned _ AND OR XOR SLL SRL SRA
module alu (in1,in2,op,out);
////////////////////////////////PARAMETERS////////////////////////////////
////////////////////////////////
parameter ADD = 4'h0 , AND = 4'h1 ,OR  = 4'h2 , XOR = 4'h3 , SUB =
4'h4 , SLT = 4'h5 , SLTU = 4'h6 ,
          SLL = 4'h7 , SRL  = 4'h8 , SRA = 4'h9 ,LUI=4'ha;

////////////////////////////////
////////////////////////////////
input signed[31:0] in1, in2;
input [3:0]op;
output reg [31:0] out;

wire [31:0] in1_1, in2_1; // unsigned input for SLU
assign in1_1=in1;
assign in2_1=in2;

always @(*) begin

    case (op)
        ADD      : begin out = in1 + in2 ;
```

```


end    // ADD
AND    : begin out = in1 & in2 ;
end    // AND
OR     : begin out = in1 | in2 ;
end    // OR
XOR    : begin out = in1 ^ in2 ;
end    // XOR
SUB    : begin out = in1 - in2 ;
end    //SUB
SLT    : begin if (in1<in2) out=1; else out =0;
end    //SLT
SLTU   : begin if ( in1_1 < in2_1 ) out=1; else out =0;
end    // SLTU
SLL    : begin out = in1    <<  in2[4:0] ;
end    // SLL
SRL    : begin out = in1_1    >>  in2[4:0] ;
end    // SRL
SRA    : begin out = in1 >>> in2[4:0] ;
end    // SRA
LUI    : begin out = in2;
        end    // LUI
default : begin out = 'bz;
end    // default

endcase

end

endmodule

```

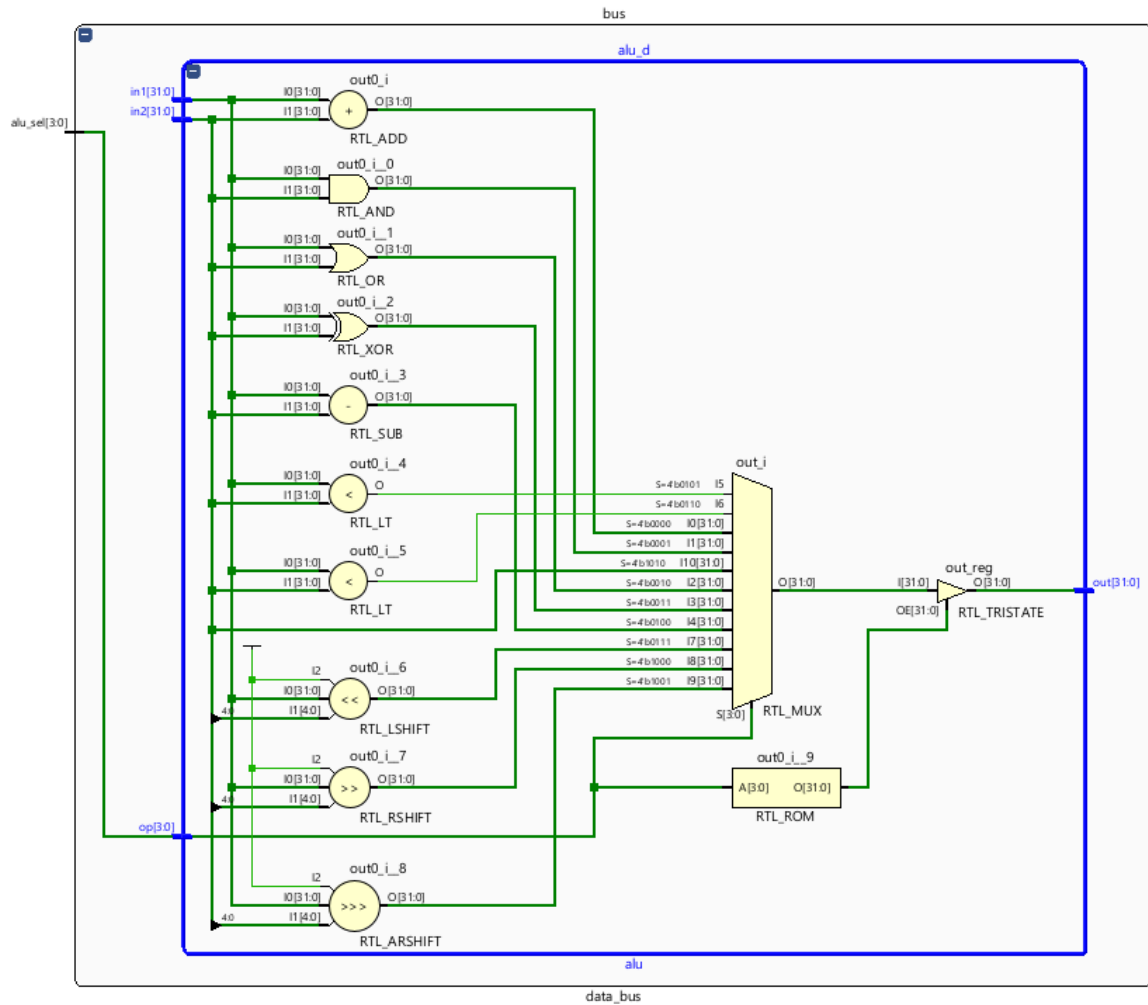Reg file: -

```



module reg_file (clk,we,w_a,r_a1,r_a2,w_d,r_d1,r_d2);
    input clk,we;
    input [4:0] w_a,r_a1,r_a2;
    input [31:0] w_d;
    output [31:0] r_d1,r_d2;

    reg [31:0] r_f [31:0];
    initial
    r_f[0]=0;
    always@(posedge clk)
    if (we)
        r_f[w_a]<=w_d;

    assign r_d1=(r_a1!=0)? r_f[r_a1] :0;
    assign r_d2=(r_a2!=0)? r_f[r_a2] :0;

endmodule

```

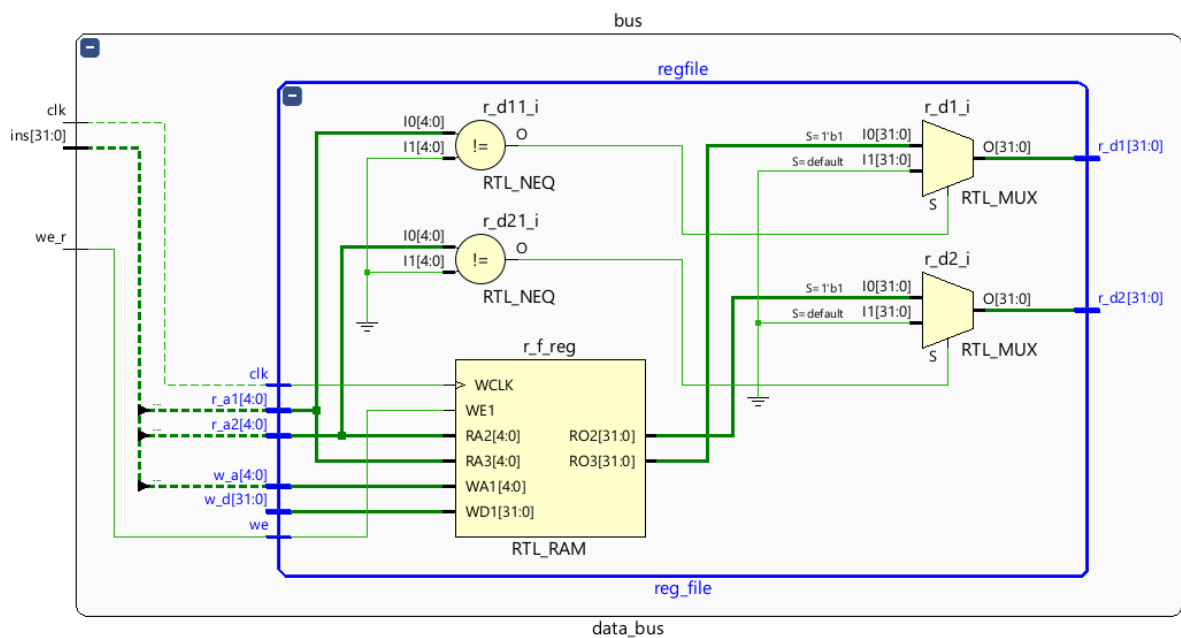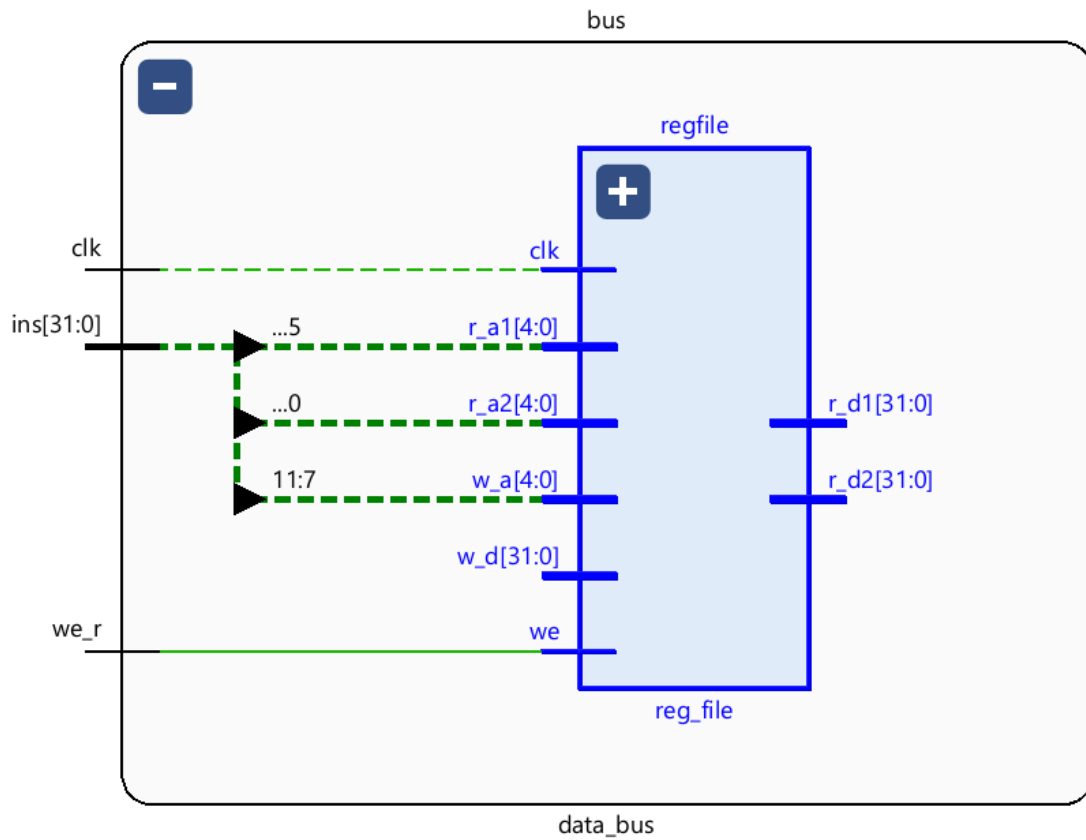

Extend (imm generation):-

```

module extend(ins,out_extend);
input signed [31:0]ins;
output reg signed [31:0] out_extend;
reg [31:0] out;

wire [6:0] opcode;
wire [2:0] funct3;
wire [6:0] funct7;
assign opcode =ins[6:0];
assign funct3 =ins[14:12];
assign funct7 =ins[31:25];

wire signed[11:0] imm_i;
assign imm_i=ins[31:20];

always @(*) begin
    out = 'bz;
    if (opcode=='h13)begin
        case (funct3)
            'b000 ,
            'b010 : out_extend=imm_i; // addi ,
slti

            'b001 : if(funct7==0) // slli
                    begin
                        out=ins[24:19];
                        out_extend=out;
                    end

            'b101 :begin if(funct7==0)
//srli          /////i*
                    begin
                        out=ins[24:19];
                        out_extend=out;
                    end
                    else
                    if(funct7=='h20)
//srai          /////i* signed
                    out_extend=ins[24:19]; end

            'b011 ,
            'b100 ,
            /// sltiu ,xori, ori,andi
            'b110 ,
            'b111 :begin
                    out=ins[31:20];
                    out_extend=out;
                end
            default : out_extend='bz;
        endcase
    end
end

```

```

        endcase
    end
    else if (opcode == 'h03')begin // i MEM
        case (funct3)
            'b000,
            'b001,
            'b010,
            'b100,
            'b101 : out_extend=ins[31:20];

            default : out_extend='bz;

        endcase
    end
    else if (opcode == 'h23')begin // S MEM
        case (funct3)
            'b000 ,
            'b001 ,
            'b010 :
out_extend={{20{1'b0}},ins[31:25],ins[11:7]}};

            default : out_extend='bz;

        endcase
    end

    else if(opcode=='h63')// Btype MEM
    begin
        case (funct3)
            'b000 ,
            'b001 ,
            'b100 ,
            'b101 ,
            'b110 ,
            'b111 : out_extend =
{{20{ins[31]}},ins[31],ins[7],ins[30:25],ins[11:8],1'b0}};
            default : out_extend = 'bz;

        endcase
    end

    end

    else if(opcode=='h67')// I type JALR
    begin
        if(funct3==0)begin
            out=ins[24:19];
            out_extend=out;
        end
    end

    else if(opcode=='h6f')// J type JAL

```

```

begin


    out_extend={{11{ins[31]}},ins[31],ins[19:12],ins[20],ins[30:21
],1'b0};

    end
    else if(opcode==7'h37)// U type          LUI
        begin
            out_extend={ins[31:12],12'b0};
        end
    else if(opcode==7'h17)// U type          AUIPC
        begin
            out_extend={ins[31:12],12'b0};
        end
    end

end

endmodule

```

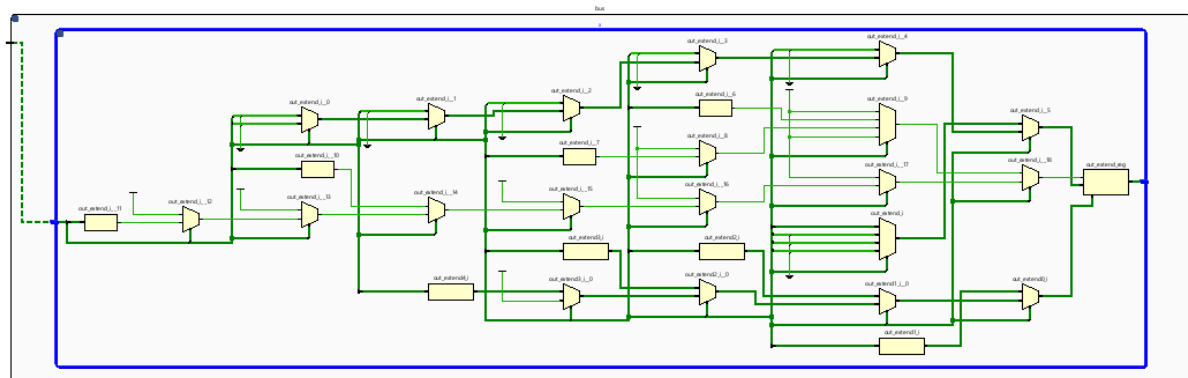

Branch comparator: -

```

module branch_comp (in1,in2,brun,breq,brlt);
input [31:0]in1,in2;
input brun;
output reg breq,brlt;

    always @(*) begin
        breq=1'bz;
        brlt=1'bz;
        if (in1==in2)
            breq=1;
        else
            breq=0;
            if(brun)begin
                if(in1<in2)
                    brlt=1;
                else
                    brlt=0;
            end
        end
    end


```

```


end
else begin
    if($signed(in1)<$signed(in2))
        brlt=1;
    else
        brlt=0;
    end
end

endmodule


```

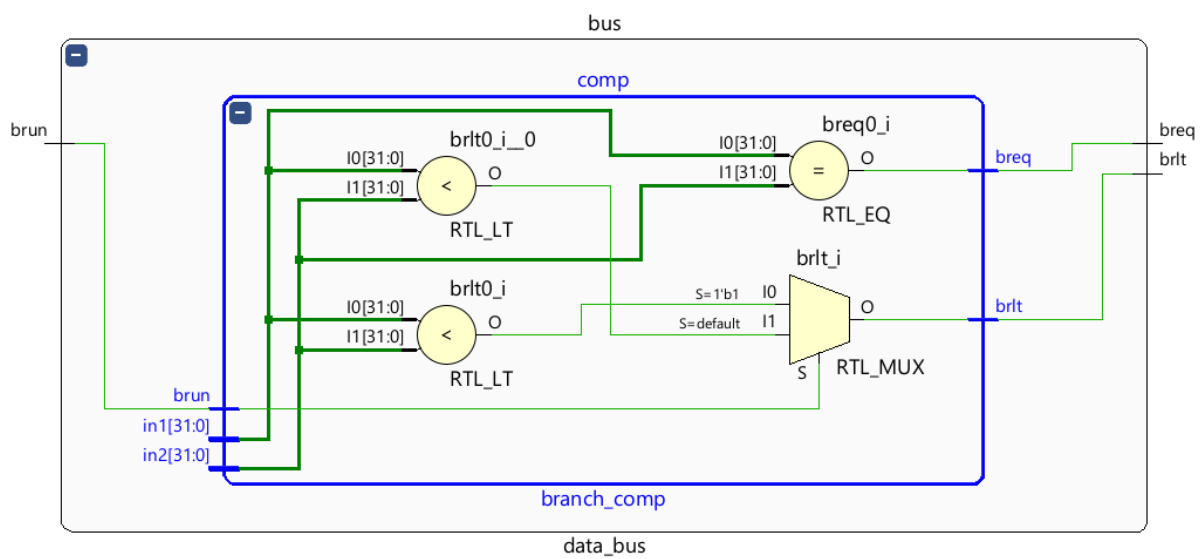

Synthesis design: -

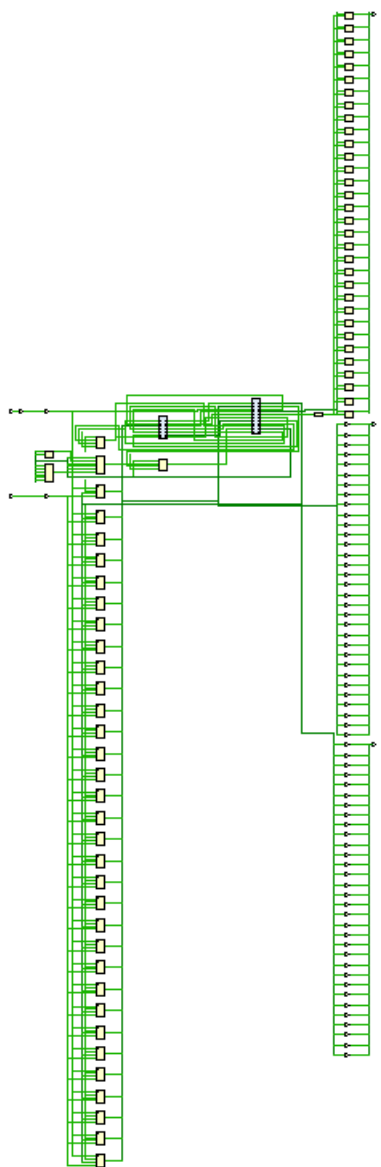

Synthesis report: -

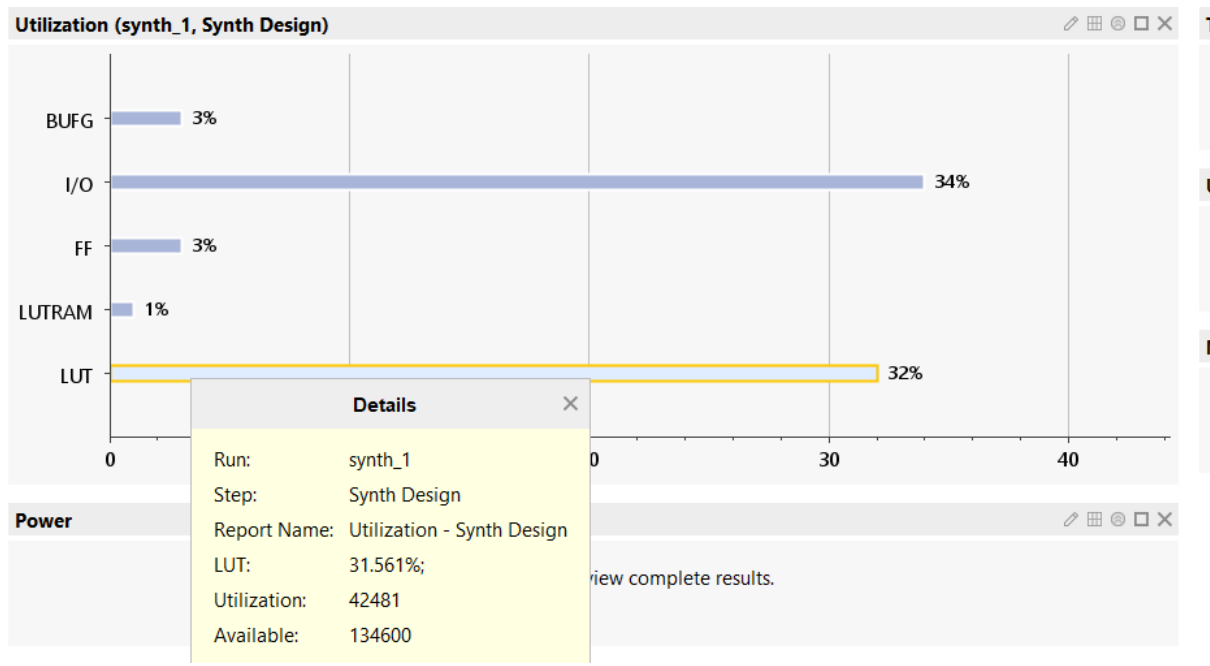

Input sample: -

```
00500113
00C00193
FF718393
0023E233
0041F2B3
004282B3
02728463
0041A233
00020463
00000293
0023A233
005203B3
402383B3
0471AA23
06002103
005104B3
008001EF
00100113
00910133
0221A023
00210063
```



```

main: addi x2, x0, 5    # x2 = 5 0 00500113
addi x3, x0, 12        # x3 = 12 4 00C00193
addi x7, x3, -9        # x7 = (12 - 9) = 3 8 FF718393
or x4, x7, x2          # x4 = (3 OR 5) = 7 C 0023E233
and x5, x3, x4         # x5 = (12 AND 7) = 4 10 0041F2B3
add x5, x5, x4         # x5 = 4 + 7 = 11 14 004282B3
beq x5, x7, end        # shouldn't be taken 18 02728863
#slt x4, x3, x4        # x4 = (12 < 7) = 0 1C 0041A233
beq x4, x0, around     # should be taken 20 00020463
addi x5, x0, 0         # shouldn't execute 24 00000293
around: #slt x4, x7, x2 # x4 = (3 < 5) = 1 28 0023A233
add x7, x4, x5         # x7 = (1 + 11) = 12 2C 005203B3
sub x7, x7, x2         # x7 = (12 - 5) = 7 30 402383B3
sw x7, 84(x3)         # [96] = 7 34 0471AA23
lw x2, 96(x0)         # x2 = [96] = 7 38 06002103
add x9, x2, x5         # x9 = (7 + 11) = 18 3C 005104B3
jal x3, end           # jump to end, x3 = 0x44 40 008001EF
addi x2, x0, 1        # shouldn't execute 44 00100113
end: add x2, x2, x9    # x2 = (7 + 18) = 25 48
sw x2, 0x20(x3)       # [100] = 25 0221A023
done: beq x2, x2, done # infinite loop 50 00210063

```

Snippets: -

[illegible]